 


Module III


Combinational Circuits

Design a logic ckt to implement the operation specified in the following table.

Input			Output
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0



 
$$X = \bar{A}BC + A\bar{B}C + ABC\bar{C}$$




Q. Develop a logic ckt with 4 input variables that will produce a '1' output when any three and only three input variables are ones.

input				Output
A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

 
$$X = \bar{A}BCD + A\bar{B}CD + AB\bar{C}D + ABC\bar{D}$$



ADDERS

 


2-bit addition

 


HA \rightarrow half adder.

Input		Output	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 Here $Sum = \bar{A}B + A\bar{B} = A \oplus B$
 $C = AB$



3-bit addition

 

A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$Sum = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$

$$C_{out} = \bar{A}BC_{in} + \bar{A}\bar{B}C_{in} + AB\bar{C}_{in} + ABC_{in}$$

$$Sum = C_{in}(\bar{A}\bar{B} + A\bar{B}) + \bar{C}_{in}(\bar{A}B + AB)$$

$$= C_{in}(A \oplus B) + \bar{C}_{in}(A \oplus B)$$

$$= C_{in}Z + \bar{C}_{in}Z$$

$$= C_{in} \oplus Z = A \oplus B \oplus C_{in}$$

$$C_{out} = \bar{A}BC_{in} + AB\bar{C}_{in} + AC_{in}(B + \bar{B})$$



$$= B(\bar{A}C_{in} + AC_{in}) + AC_{in}$$

$$= B(A \oplus C_{in}) + AC_{in}$$


OR

$$C_{out} = C_{in}(\bar{A}B + A\bar{B}) + AB(\bar{C}_{in} + C_{in})$$


$$= C_{in}(A \oplus B) + AB$$

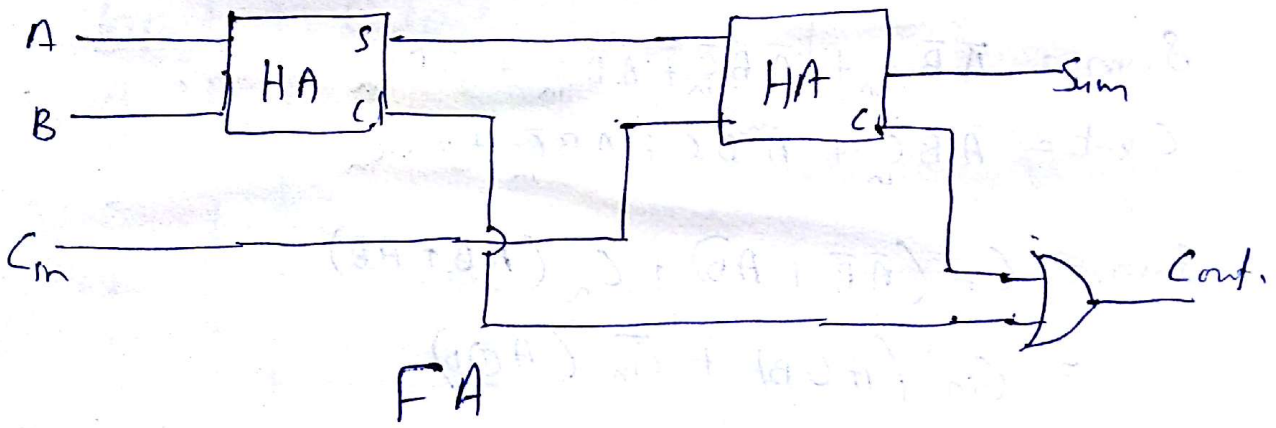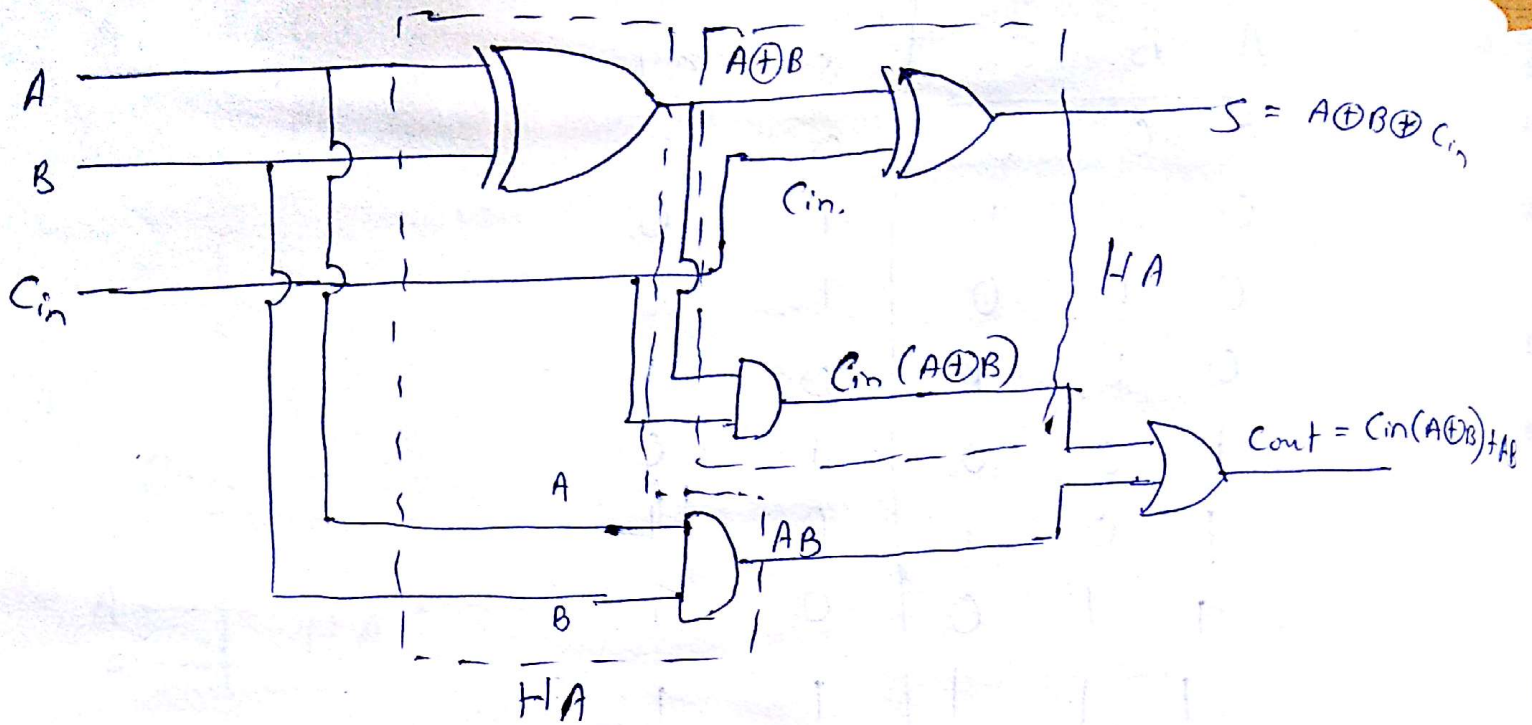


Parallel binary adder.

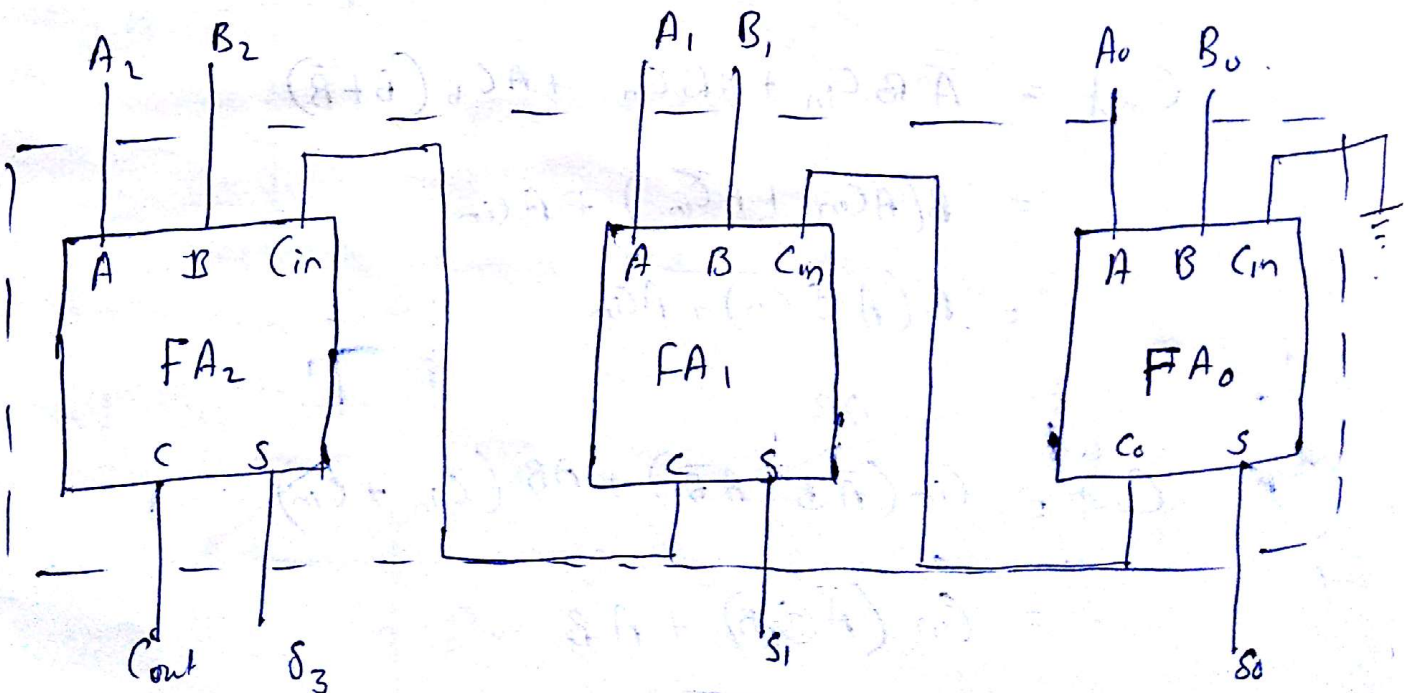

 Block diagram of 3 bit parallel binary adder,



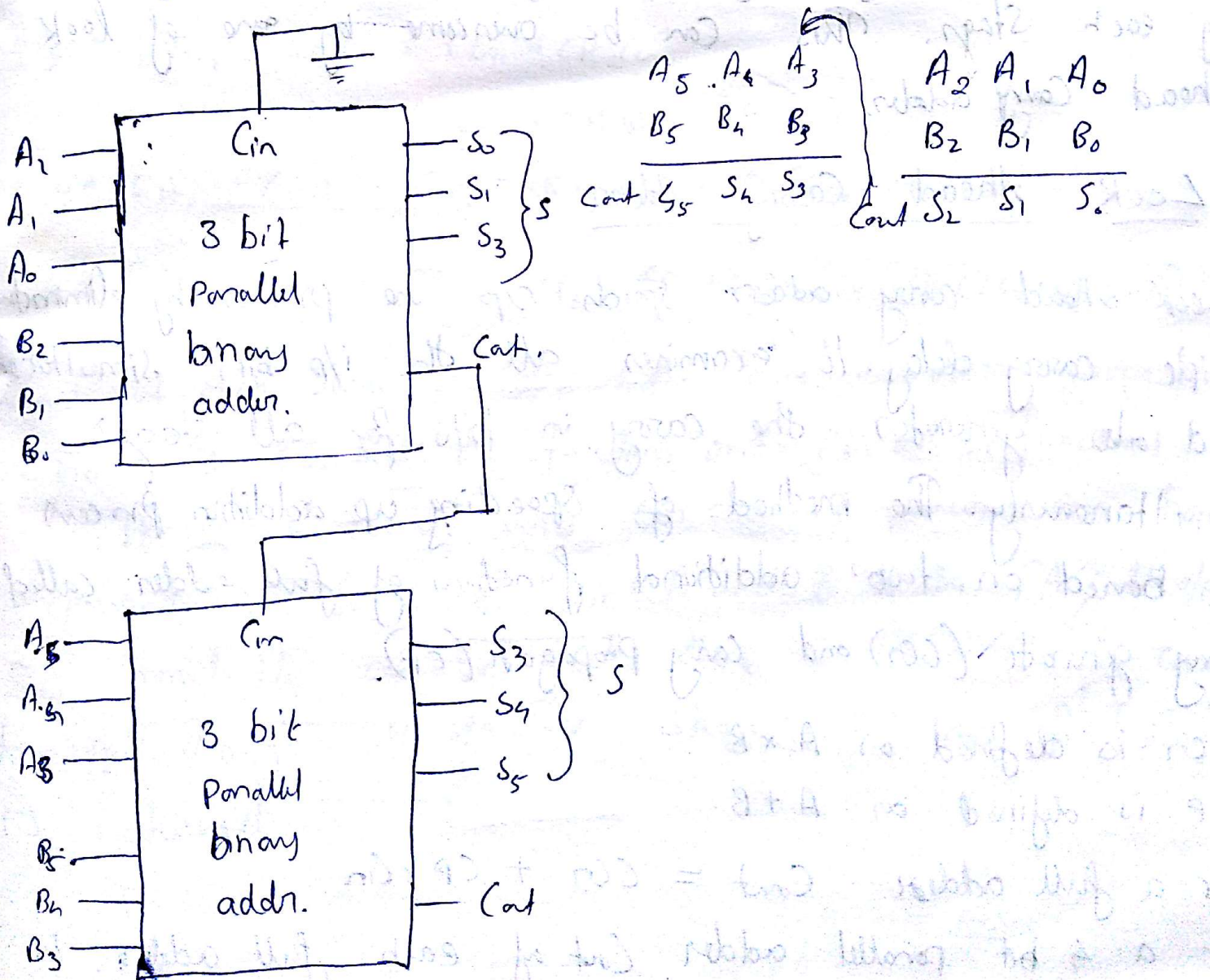Q. Show how ~~two~~ 3 bit parallel adder can be connected to form a 6 bit parallel adder.



Propagation delay - The first full adder performs addition.
→ The carryout is given to 2nd full adder. The 2nd full adder performs addition only when Cout of 1st FA is given to Cin of 2nd FA.

In parallel adders discussed the carryout of each stage is connected to the carry in of the next stage. The sum and carryouts of any stage cannot be produced until the i/p carry occurs, which leads to time delay. The total delay varies depending on carries produced by each stage. This can be overcome by use of look ahead carry adder.

Look Ahead Carry Adder

Look ahead carry adder speeds up the process by eliminating ripple carry delay. It examines all the i/p bits simultaneously and also generates the carry in bits for all stages simultaneously. The method of speeding up addition process is based on two additional functions of full adder called carry generate (CG) and carry propagate (CP).


CG is defined as $A \times B$

CP is defined as $A + B$.

For a full adder $C_{out} = CG + CP \times C_{in}$

For a 4 bit parallel adder Cout of each full adder is depended on its CG, CP and its Cin. CG and CP for

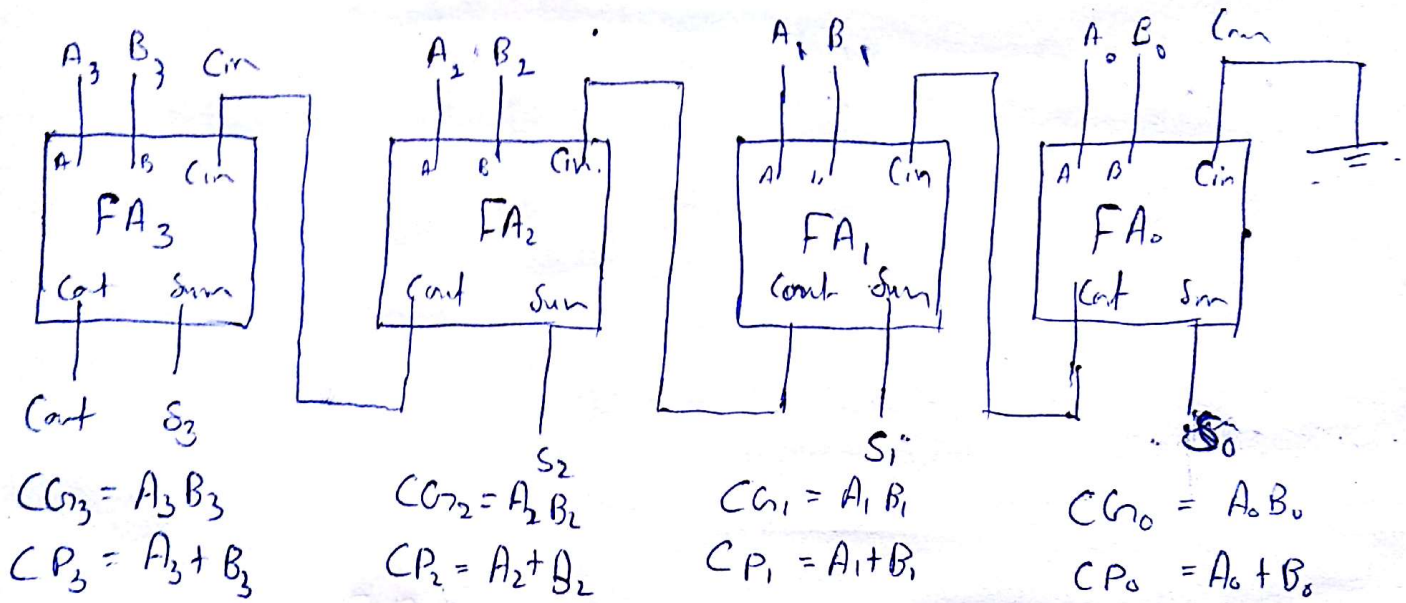each stage are immediately available as soon as input bits are applied to each adder.



1st FA, $C_{out0} = C_{G0} + C_{P0} C_{in0}$

2nd FA, $C_{out1} = C_{G1} + C_{P1} C_{in1}$
 $= C_{G1} + C_{P1} (C_{G0} + C_{P0} C_{in0})$

3rd FA, $C_{out2} = C_{G2} + C_{P2} \times [C_{G1} + C_{P1} (C_{G0} + C_{P0} C_{in0})]$

4th FA, $C_{out3} = C_{G3} + C_{P3} \times [C_{G2} + C_{P2} \times (C_{G1} + C_{P1} (C_{G0} + C_{P0} C_{in0}))]$

Carry of each stage is dependent only in initial carry in C_{in0} . Its C_G and C_P functions and C_G and C_P functions of preceding stage. Since C_G and C_P functions can be expressed in terms of i/p, A and B to the FA, all o/p's are immediately available and there is no need for carry to ripple through all of these stages before the final stage is achieved.

SUBTRACTORS


Half Subtractors

Inputs		Outputs	
A	B	d	b
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\begin{array}{r} \sim b \\ 10 \\ - 1 \\ \hline 1 \end{array}$$

$$d = \bar{A}B + A\bar{B} = A \oplus B$$

$$b = \bar{A}B$$

 

Full Subtractor

Inputs			Outputs	
A	B	b _{in}	d	b _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\begin{aligned} d &= \bar{A}\bar{B}b_{in} + \bar{A}B\bar{b}_{in} + A\bar{B}\bar{b}_{in} + ABb_{in} \\ &= \bar{A}(\bar{B}b_{in} + B\bar{b}_{in}) + A(\bar{B}\bar{b}_{in} + Bb_{in}) \\ &= \bar{A}(B \oplus b_{in}) + A(\bar{B} \oplus b_{in}) \\ &= A \oplus (B \oplus b_{in}) \end{aligned}$$

$$B \oplus b_{in} = Z$$


$$\therefore d = \bar{A}Z + A\bar{Z} = A \oplus Z = A \oplus (B \oplus b_{in})$$

$$\begin{aligned} b_{out} &= \bar{A}\bar{B}b_{in} + \bar{A}B\bar{b}_{in} + \bar{A}Bb_{in} + ABb_{in} \\ &= \bar{A}(\bar{B}b_{in} + B\bar{b}_{in}) + B(\bar{A}b_{in} + Ab_{in}) \\ &= \bar{A}\bar{B} + (A \odot B)b_{in} \end{aligned}$$


Code Converters

Code converters are logic converters circuits whose inputs are bit patterns representing no.s in one code and whose outputs are corresponding representation in a different code.

 Q. Design and implement a 4 bit binary to Gray code converter.



	i/p				o/p				
	B ₃	B ₂	B ₁	B ₀	G ₃	G ₂	G ₁	G ₀	
0	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1	1
2	0	0	1	0	0	0	1	1	3
3	0	0	1	1	0	0	1	0	2
4	0	1	0	0	0	1	0	0	6
5	0	1	0	1	0	1	0	1	7
6	0	1	1	0	0	1	0	1	5
7	0	1	1	1	0	1	0	0	4
8	1	0	0	0	1	1	0	0	12
9	1	0	0	1	1	1	0	0	13
10	1	0	1	0	1	1	1	1	15
11	1	0	1	1	1	1	1	0	14
12	1	1	0	0	1	0	1	0	10
13	1	1	0	1	1	0	1	1	11
14	1	1	1	0	1	0	0	1	9
15	1	1	1	1	1	0	0	0	8

 

$$G_3 = B_3 \bar{B}_2 \bar{B}_1 \bar{B}_0 + B_3 \bar{B}_2 \bar{B}_1 B_0 + B_3 \bar{B}_2 B_1 \bar{B}_0 + B_3 \bar{B}_2 B_1 B_0 +$$

$$B_3 B_2 \bar{B}_1 \bar{B}_0 + B_3 B_2 \bar{B}_1 B_0 + B_3 B_2 B_1 \bar{B}_0 + B_3 B_2 B_1 B_0$$

Using K-MAP

		$B_1 \bar{B}_0$	$\bar{B}_1 \bar{B}_0$	$B_1 B_0$	$\bar{B}_1 B_0$
$B_3 B_2$					
$\bar{B}_3 B_2$					
$B_3 \bar{B}_2$	1	1	1	1	
$\bar{B}_3 \bar{B}_2$	1	1	1	1	

$$\therefore G_3 = B_3$$

$$G_2 = \bar{B}_3 B_2 \bar{B}_1 \bar{B}_0 + \bar{B}_3 B_2 \bar{B}_1 B_0 + \bar{B}_3 B_2 B_1 \bar{B}_0 + \bar{B}_3 B_2 B_1 B_0 + B_3 \bar{B}_2 \bar{B}_1 \bar{B}_0$$

$$+ B_3 \bar{B}_2 \bar{B}_1 B_0 + B_3 \bar{B}_2 B_1 \bar{B}_0$$

		$B_1 \bar{B}_0$	$\bar{B}_1 \bar{B}_0$	$B_1 B_0$	$\bar{B}_1 B_0$
$\bar{B}_3 \bar{B}_2$					
$\bar{B}_3 B_2$	1	1	1	1	
$B_3 B_2$					
$B_3 \bar{B}_2$	1	1	1	1	

$$G_2 = \bar{B}_3 B_2 + B_3 \bar{B}_2$$

$$= B_3 \oplus B_2$$


G_1 K-MAP

		$B_1 \bar{B}_0$	$\bar{B}_1 \bar{B}_0$	$B_1 B_0$	$\bar{B}_1 B_0$
$\bar{B}_3 \bar{B}_2$				1	1
$\bar{B}_3 B_2$	1	1			
$B_3 B_2$	1	1			
$B_3 \bar{B}_2$			1	1	

$$G_1 = B_2 \bar{B}_1 + \bar{B}_2 B_1$$

$$= B_2 \oplus B_1$$


Similarly $G_0 = B_1 \oplus B_0$.

 

Q. Design and Implement. 4 bit binary to BCD Converter.
i/p o/p.

B_3	B_2	B_1	B_0	A	B	C	D	E
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	1
0	0	1	0	0	0	0	1	0
0	0	1	1	0	0	0	1	1
0	1	0	0	0	0	1	0	0
0	1	0	1	0	0	1	0	1
0	1	1	0	0	0	1	1	0
0	1	1	1	0	0	1	1	1
1	0	0	0	0	1	0	0	0
1	0	0	1	0	1	0	0	1
1	0	1	0	1	0	0	0	0
1	0	1	1	1	0	0	0	1
1	1	0	0	1	0	0	1	0
1	1	0	1	1	0	0	1	1
1	1	1	0	1	0	0	0	0
1	1	1	1	1	0	1	0	1

A_1 using K-Map.

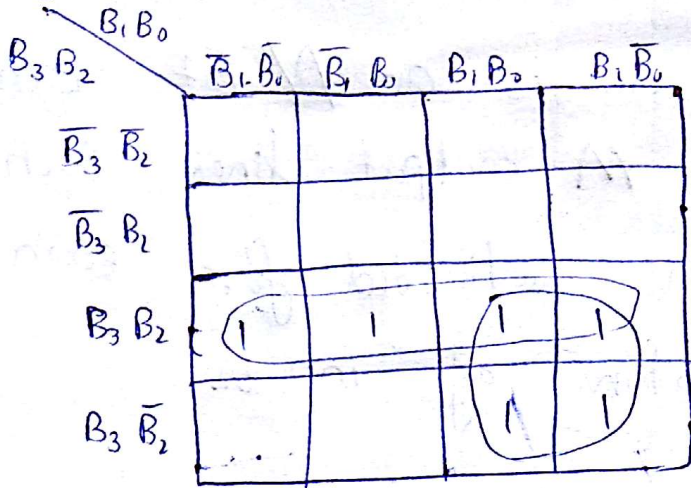

$$A = B_3 B_2 + B_3 B_1$$


Similarly

$$B = B_3 \bar{B}_2 B_1$$

$$C = \bar{B}_3 B_2 + B_2 B_1$$

$$D = B_3 B_2 \bar{B}_1 + \bar{B}_3 B_1$$

$$E = B_0$$

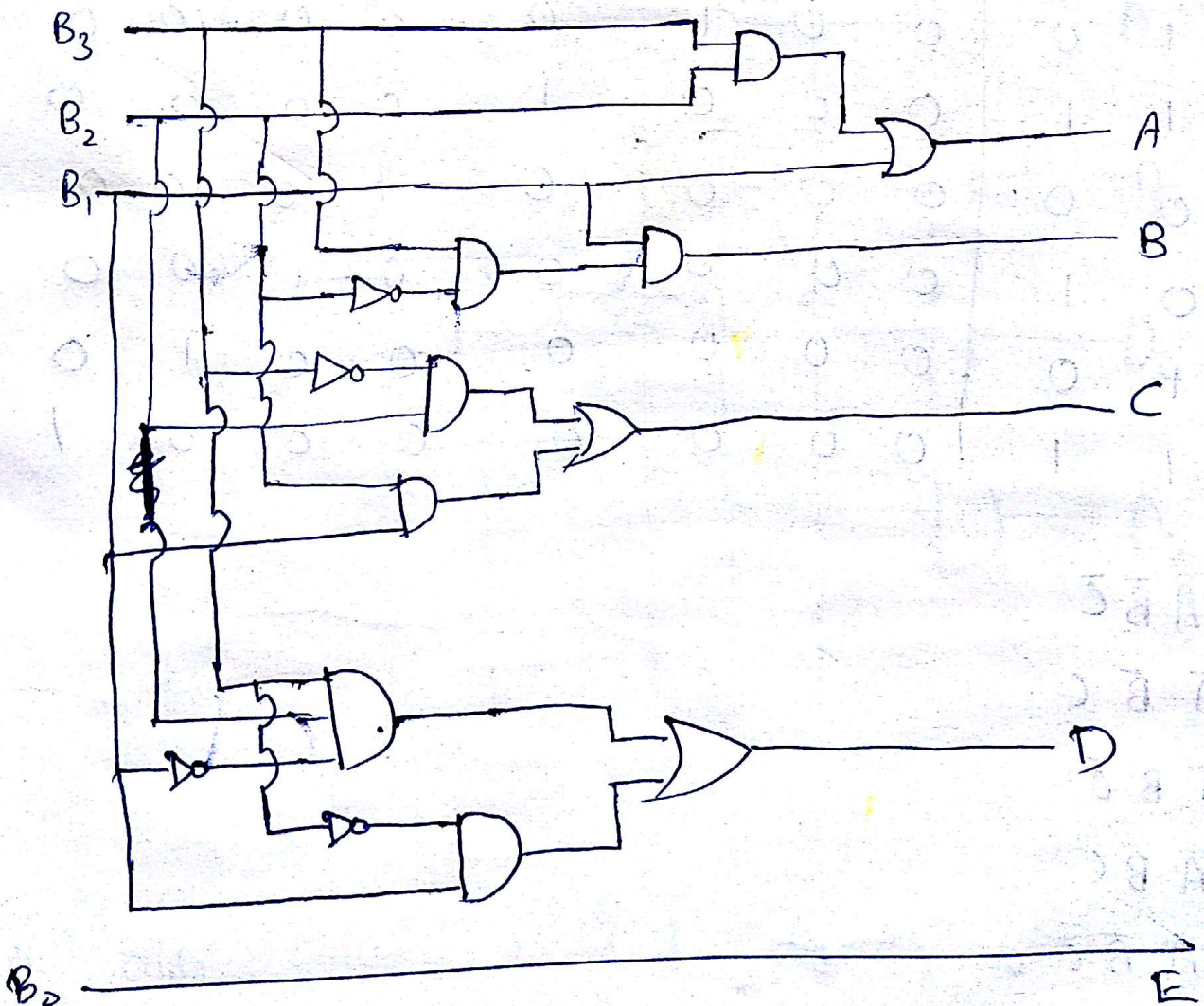

Decoders

Logic circuits that converts an N bit binary input code into M output lines such that only one output line is activated for each one of the possible combinations of inputs.

3-to-8 Decoder

3 i/p's and 8 o/p's with 7 low and 1 high.

inputs			ACTIVE HIGH							
A	B	C	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$D_0 = \bar{A} \bar{B} \bar{C}$$

$$D_1 = \bar{A} \bar{B} C$$

$$D_2 = \bar{A} B \bar{C}$$


$$D_3 = \bar{A} B C$$

$$D_4 = A \bar{B} \bar{C}$$

$$D_5 = A \bar{B} C$$

$$D_6 = A B \bar{C}$$

$$D_7 = A B C$$

 


It is also called 1 of 8 decoder since one of 8 i's activate.

Enable Inputs

They are used to control the operation of a decoder. Eg:- In a 3-to-8 decoder is a common enable input is connected to the 4th input of each gate, a particular output as determined by A, B and C will go high only when the enabled line is held high. If the Enable is low all outputs will be found to low regardless of the levels at A, B and C inputs.

Eg:-

 

ACTIVE LOW 3-to-8 Decoder

Here to obtain active low 3-to-8 decoder we replace the AND gates by NAND gate.

Eg: Truth table.

Inputs			Outputs							
A	B	C	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	0	1	1	1	1	1	1	1
0	0	1	1	0	1	1	1	1	1	1
0	1	0	1	1	0	1	1	1	1	1
0	1	1	1	1	1	0	1	1	1	1

Assignment Q. Active LOW 4-to-16 Decoder.

4 bit BCD - to - Decimal decoder

Inputs														
A	B	C	D		D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	D ₈	D ₉
0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	1	0	0	0	0	0	0	0
3	0	0	1	1	0	0	0	1	0	0	0	0	0	0
4	0	1	0	0	0	0	0	0	1	0	0	0	0	0
5	0	1	0	1	0	0	0	0	0	1	0	0	0	0
6	0	1	1	0	0	0	0	0	0	0	1	0	0	0
7	0	1	1	1	0	0	0	0	0	0	0	1	0	0
8	1	0	0	0	0	0	0	0	0	0	0	0	1	0
9	1	0	0	1	0	0	0	0	0	0	0	0	0	1
10	1	0	0	0										

Only 10 combinations are possible else others are invalid.
It is also called 4-to-10 / 1-of-10 decoder.

$$D_0 = \bar{A} \bar{B} \bar{C} \bar{D}$$

$$D_8 = A \bar{B} \bar{C} \bar{D}$$

$$D_1 = \bar{A} \bar{B} \bar{C} D$$

$$D_9 = A \bar{B} \bar{C} D$$

$$D_2 = \bar{A} \bar{B} C \bar{D}$$


$$D_3 = \bar{A} \bar{B} C D$$


$$D_4 = \bar{A} B \bar{C} \bar{D}$$

$$D_5 = \bar{A} B \bar{C} D$$

$$D_6 = \bar{A} B C \bar{D}$$



$$D_7 = \bar{A} B C D$$

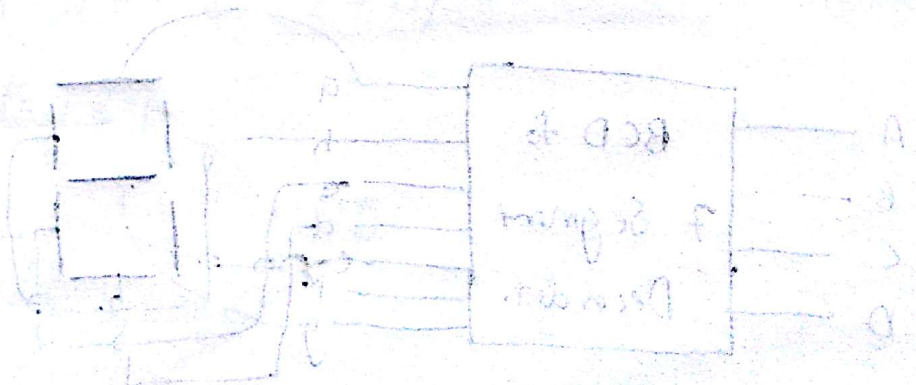

 


BCD to 7 segment

 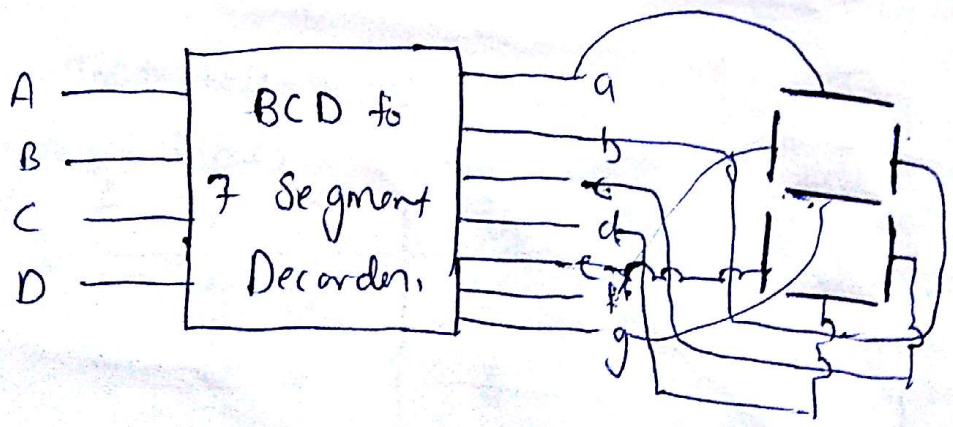This accepts BCD code and provides o/p to energise 7 segment display devices in order to produce a decimal readout. A 7 segment display is normally used for displaying any one of the decimal digits 0 to 9. It is composed of 7 light emitting sections designated as letters ~~from~~ a to g. By illuminating various numbers from 0 to 9 can be obtained.



	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	1
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1

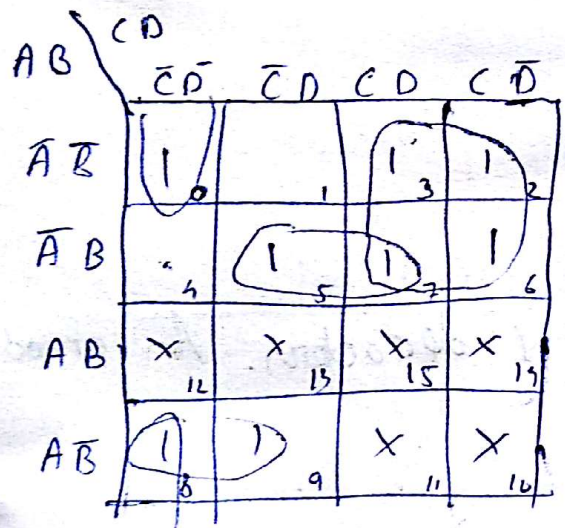

$$a = A + C + B \oplus D$$

$$a = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D$$

Similarly

$$b = \bar{B} + C \oplus D$$

$$c = B + \bar{C} + D$$

$$d = A + \bar{C}\bar{D} + B \oplus (C + \bar{D})$$

$$e = \bar{B}\bar{D} + C\bar{D}$$

$$f = A + \bar{C}\bar{D} + B\bar{C} + B\bar{D}$$

$$g = A + C\bar{D} + B \oplus C$$

ENCODERS

They perform the reverse operation of decoders. An encoder has M inputs and N o/p's.


Octal - to - Binary Encoder (8-to-3 Encoder)

I/P	A	B/P	C
D_0	0	0	0
D_1	0	0	1
D_2	0	1	0
D_3	0	1	1
D_4	1	0	0
D_5	1	0	1
D_6	1	1	0
D_7	1	1	1

$$A = D_4 + D_5 + D_6 + D_7$$

$$B = D_2 + D_3 + D_6 + D_7$$

$$C = D_1 + D_3 + D_5 + D_7$$

 

Decimal-to-BCD Encoder


input	Output			
	A	B	C	D
D_0	0	0	0	0
D_1	0	0	0	1
D_2	0	0	1	0
D_3	0	0	1	1
D_4	0	1	0	0
D_5	0	1	0	1
D_6	0	1	1	0
D_7	0	1	1	1
D_8	1	0	0	0
D_9	1	0	0	1

$$A = D_8 + D_9$$

$$B = D_4 + D_5 + D_6 + D_7$$

$$C = D_2 + D_3 + D_6 + D_7$$


$$D = D_1 + D_3 + D_5 + D_7 + D_9$$

 

MULTIPLEXERS (MUX) / Data selectors (Many to One)


Multiplexer is a logic ckt that accepts several data i/ps and allows only one of them at a time to get through the o/p. For N input lines, the no. of select lines m should be such that $2^m = N$.

2x1 MUX,

 


S	Y
0	D_0
1	D_1

$$Y = D_0 \bar{S} + D_1 S$$

 


4x1 MUX

 


S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3
 
$$Y = D_0 \bar{S}_1 \bar{S}_0 + D_1 \bar{S}_1 S_0 + D_2 S_1 \bar{S}_0 + D_3 S_1 S_0$$




8x1 MUX

 


S_2	S_1	S_0	Y
0	0	0	D_0
0	0	1	D_1
0	1	0	D_2
0	1	1	D_3
1	0	0	D_4
1	0	1	D_5
1	1	0	D_6
1	1	1	D_7
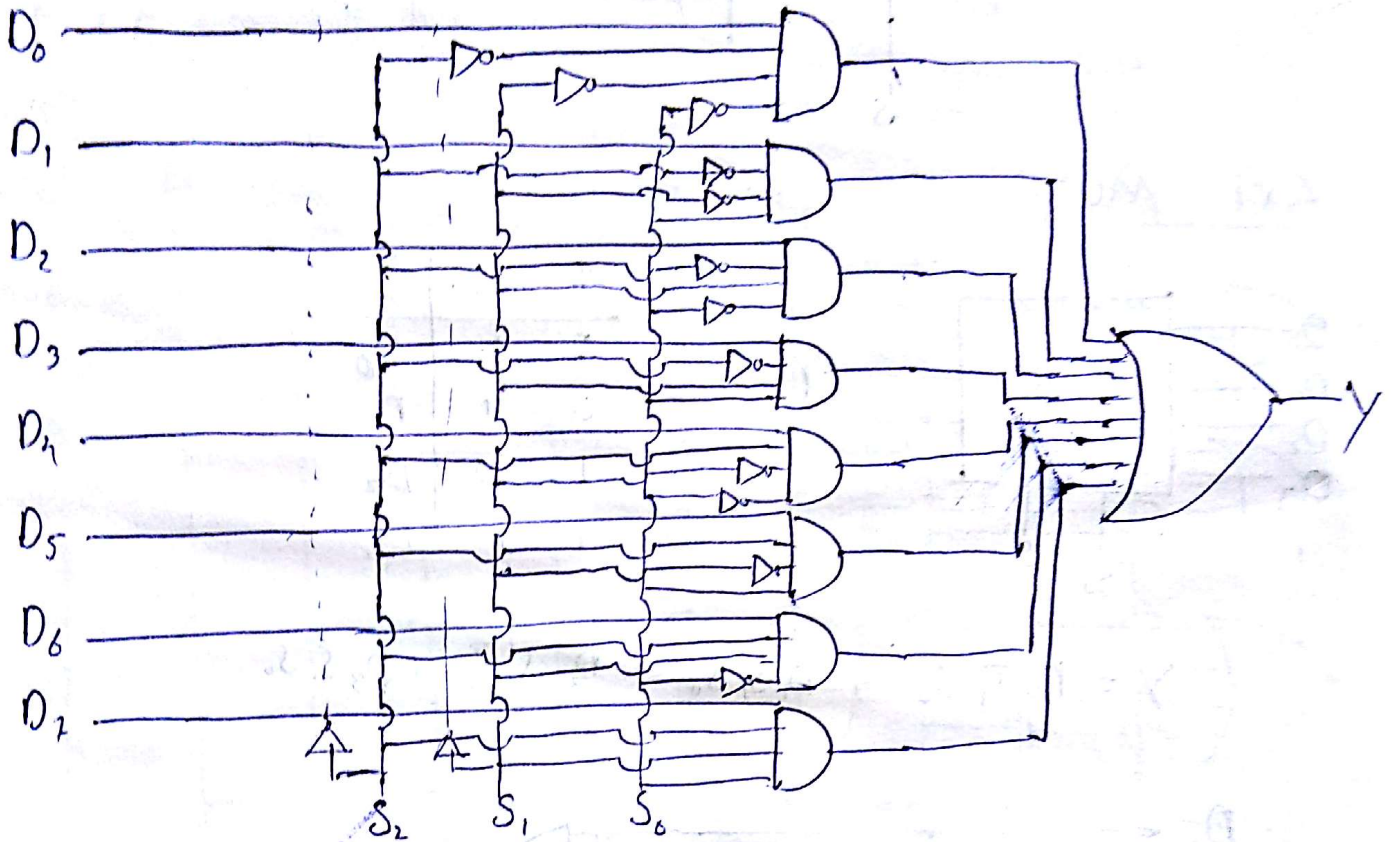
$$Y = D_0 \bar{S}_0 \bar{S}_1 \bar{S}_2 + D_1 \bar{S}_2 \bar{S}_1 S_0 + D_2 \bar{S}_2 S_1 \bar{S}_0 + D_3 \bar{S}_2 S_1 S_0 + D_4 S_2 \bar{S}_1 \bar{S}_0 + D_5 S_2 S_1 S_0 + D_6 S_2 S_1 \bar{S}_0 + D_7 S_2 S_1 S_0$$



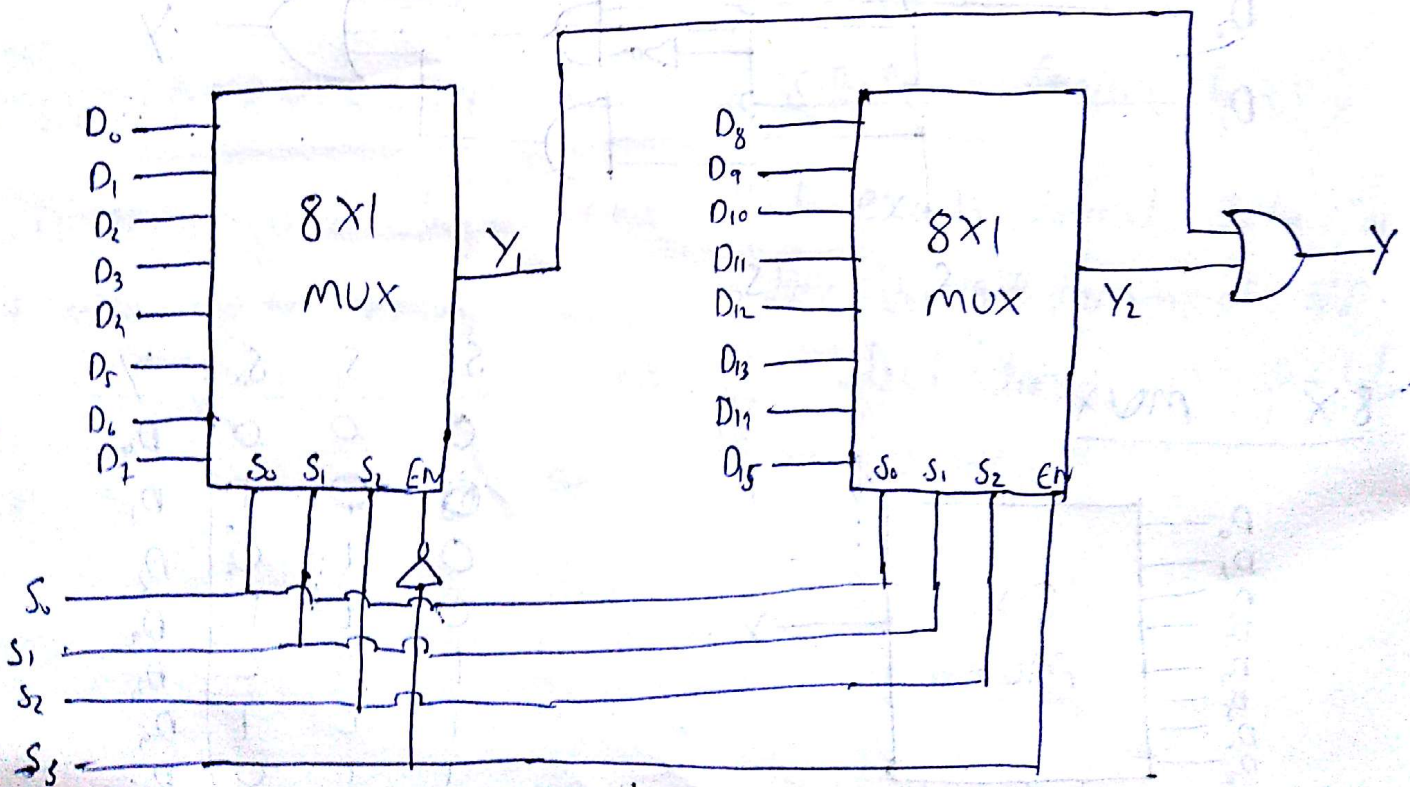Q. Design and implement a 16x1 MUX with two 8x1 MUX



S_3	S_2	S_1	S_0	
0	0	0	0	D_0
0	0	0	1	D_1
⋮	⋮	⋮	⋮	
0	1	1	1	D_7
<hr/>				
1	0	0	0	D_8
1	0	0	1	D_9
⋮	⋮	⋮	⋮	
1	1	1	1	D_{15}

S_3 is zero in the part which is given to 1st MUX through NOT.


To select one of the 16 inputs, 4 select lines (S_3, S_2, S_1, S_0) are required. Amongst the 4 select lines, the least significant 3 select lines are connected with the select i/p's of both the MUX. Most significant bit S_3 is ~~directly~~ connected to ENABLE of MUX₁ through an inverter and directly connected to ENABLE of MUX₂. When $S_3 = 0$, MUX one is enabled, D_0 to D_7 is selected. When $S_3 = 1$, MUX one is disabled, MUX 2 is enabled and i/p's D_8 to D_{15} are selected. The outputs of MUX₁ and MUX₂ are OR gated to generate o/p Y .

Application of MULTIPLEXERS


1. Data routing or data selecting.
2. Logic function generator.
3. Control sequencer.
4. Parallel to serial converter.

Demultiplexers

one to many.
data detectors.

 

1 X 4 DeMUX

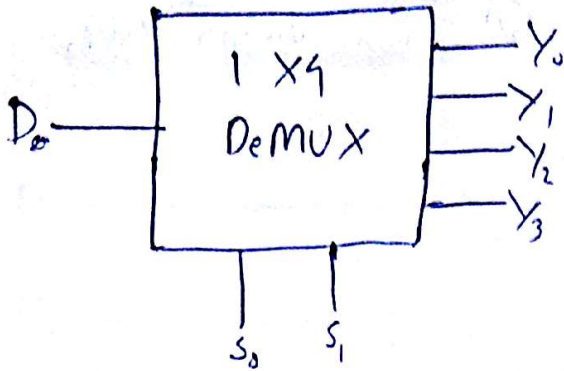

S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

$$Y_0 = D \bar{S}_1 \bar{S}_0$$

$$Y_1 = D \bar{S}_1 S_0$$

$$Y_2 = D S_1 \bar{S}_0$$

$$Y_3 = D S_1 S_0$$

